
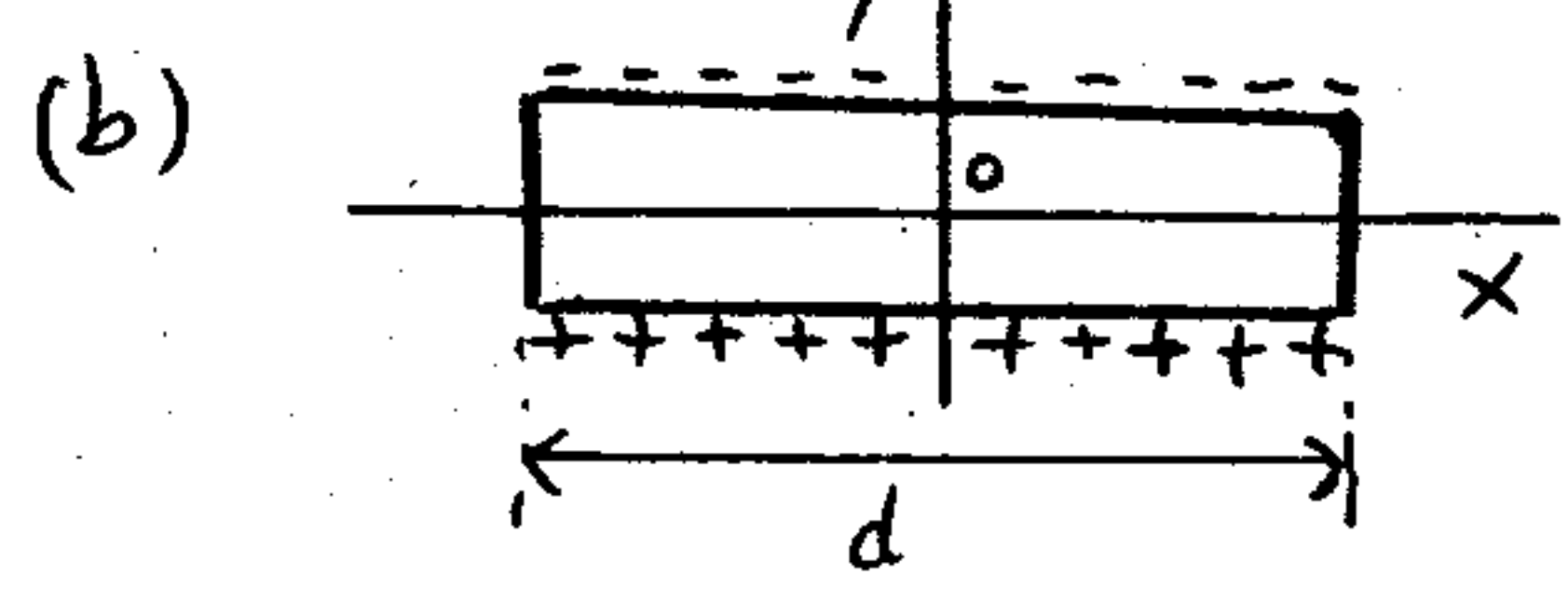


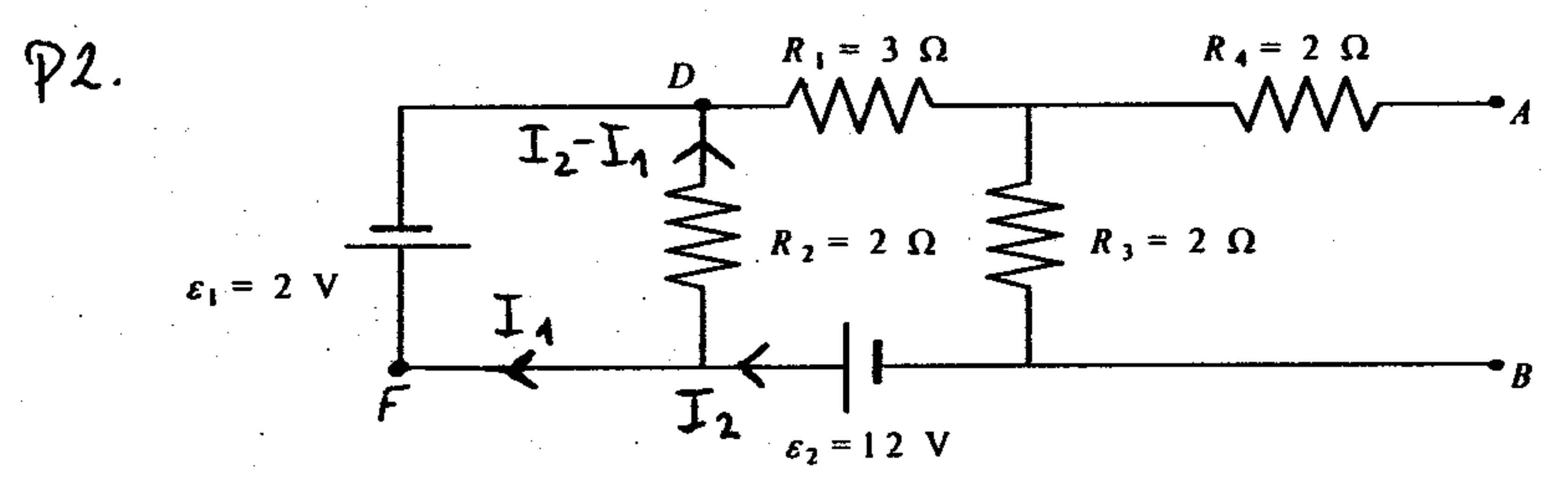P1. (a) $\vec{E} = -400 \hat{j} \frac{N}{C}$; $V_B - V_A = -\int_A^B \vec{E} \cdot d\vec{\ell} = -\int_A^B (E_x dx + E_y dy + E_z dz) = -\int_A^C E_y dy - \int_C^B E_y dy = 400 [y]_{-0.6}^{0.7} + 400 [y]_{0.7}^0 = 520 V$ $V_B > V_A$



(b) En equilibri, $\vec{E} = -\vec{E}_{2\text{ plans}} \Rightarrow +400 \hat{j} = +\frac{\sigma}{\epsilon_0} \hat{j} \Rightarrow \sigma = 400 \epsilon_0 = 3.536 \text{ nC/m}^2$
 $q = \sigma \cdot S = \sigma \pi \left(\frac{d}{2}\right)^2 = 3.9 \text{ pC}$; $\vec{E}_{\text{interior}} = 0$; $\vec{E}_{\text{exterior}} = \vec{E}$




(a) Equacions del circuit:
$$\left. \begin{aligned} \epsilon_1 &= R_2 (I_2 - I_1) \\ \epsilon_2 &= R_2 (I_2 - I_1) + (R_1 + R_3) I_2 \end{aligned} \right\} \Rightarrow$$

$$\Rightarrow I_1 = 1 A, I_2 = 2 A, I_2 - I_1 = 1 A$$

 (b) $V_D - V_B = (R_1 + R_3) I_2 = 10 V$
 (c) $V_{Th} = V_A - V_B = I_2 R_3 = 4 V$
 $R_{Th} = (R_1 \parallel R_3) + R_4 = 3.2 \Omega$, donat que es curtcircuita R_2

(d) $Q = q(\infty) = C(V_A - V_B) = C \cdot V_{Th} = 16 \mu C$
 on $q(t) = Q(1 - e^{-t/RC}) = 16 \cdot 10^{-6} (1 - e^{-t/12.8 \cdot 10^{-6}}) C \Rightarrow 0.9 Q = Q(1 - e^{-t/RC}) \Rightarrow t = -RC \ln 0.1 = 2.95 \cdot 10^{-5} s$

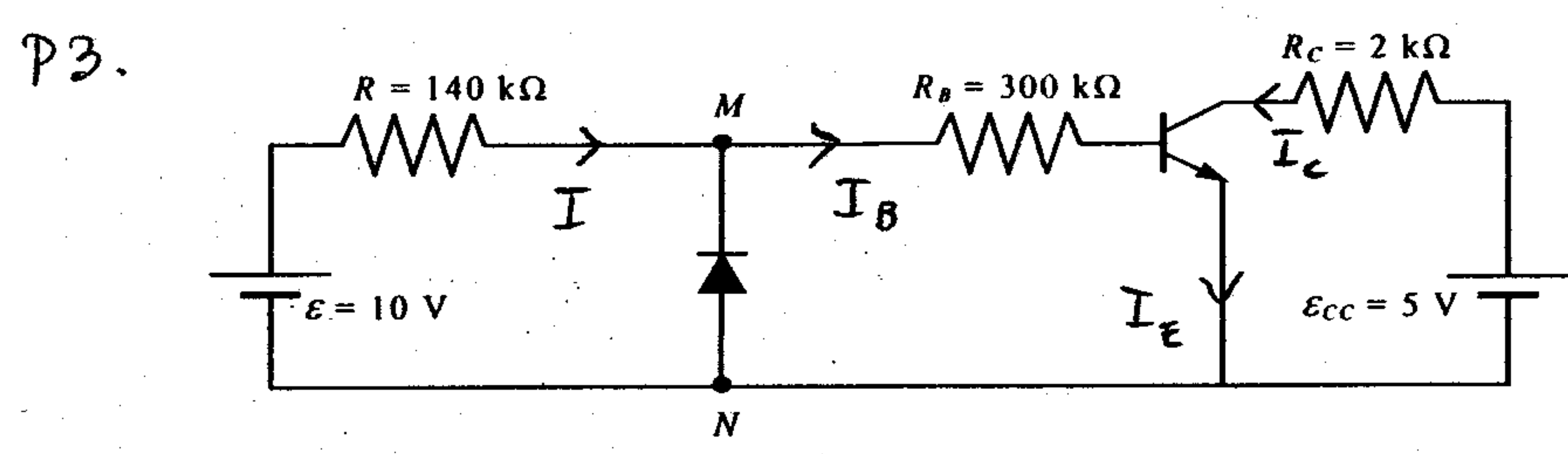(e) $P_{\text{sub.}} = (V_D - V_F) I_1 + (V_F - V_B) I_2 = -\epsilon_1 I_1 + \epsilon_2 I_2 = 22 W$



(a) Diode en polarització inversa, $I_D = 0$; $I_B = I = 21.1 \mu A$

$$\left. \begin{aligned} \epsilon &= IR + V_M - V_N \\ V_M - V_N &= I_B R_B + V_{BE} \end{aligned} \right\} I = \frac{\epsilon - V_{BE}}{R + R_B} = 21.1 \mu A$$

$$\text{Suposem zona activa... } I_C = \beta I_B = 3.17 \text{ mA} \Rightarrow V_{CE} = \epsilon_{cc} - I_C R_C = 5 - 3.17 \cdot 2 = -1.34 V \downarrow$$

 En saturació: $V_{CE} = 0.2 V$; $I_C = \frac{\epsilon_{cc} - V_{CE}}{R_C} = 2.4 \text{ mA}$
 $I_E = I_B + I_C = 2.42 \text{ mA}$ 2. saturació

(b) Si invertim el díode, fa que $V_M - V_N = V_f = 0.6 V \Rightarrow$
 \Rightarrow es curtcircuita la part d'entrada del transistor $\Rightarrow I_B = 0, I_D = I = \frac{\epsilon - V_f}{R} = 67.1 \mu A$
 $\Rightarrow I_C = 0, I_E = 0, V_{CE} = 5 V, V_{BE} = V_M - V_N = 0.6 V$